 


ساختار و زبان کامپیوتر


فصل ششم

سازمان حافظه




Computer Structure and Machine Language

Chapter Six Memory Organization

 

Logic and Computer Design Fundamentals

Fifth Edition

 

Chapter 7:

Memory Basics

This work is protected by United States copyright laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted. The work and materials from it should never be made available to students except by instructors using the accompanying text in their classes. All recipients of this work are expected to abide by these restrictions and to honor the intended pedagogical purposes and the needs of other instructors who rely on these materials.



Copyright © 2016, 2008, 2004 Pearson Education, Inc. All Rights Reserved

Contents

- *Memory Definitions*
- *Random Access Memory*
 - *SRAM Integrated Circuits*
 - *Array of SRAM ICs*
 - *DRAM Integrated Circuits*
- *Read Only Memory*



Memory

- A collection of cells capable of storing binary information
- Contains electronic circuits for storing and retrieving the information
- Used in many different parts of a computer, providing **temporary** or **permanent** storage for substantial amounts of **binary** information



Memory Organization

Key Characteristics

Location Internal (e.g., processor registers, cache, main memory) External (e.g., optical disks, magnetic disks, tapes)	Performance Access time Cycle time Transfer rate
Capacity Number of words Number of bytes	Physical Type Semiconductor Magnetic Optical Magneto-optical
Unit of Transfer Word Block	Physical Characteristics Volatile/nonvolatile Erasable/nonerasable
Access Method Sequential Direct Random Associative	Organization Memory modules

Fall 2021
Memory Definitions
6

Two types of memories are used in various parts of a computer: *random-access memory* (RAM) and *read-only memory* (ROM).

RAM accepts new information for storage to be available later for use.

The process of storing new information in memory is referred to as a *memory write* operation.

The process of transferring the stored information out of memory is referred to as a *memory read* operation.

RAM can perform both the write and the read operations, whereas ROM performs only read operations.

Memory units that lose stored information when power is turned off are said to be *volatile*.

RAMs are volatile while ROMs are *nonvolatile*.

Direct access: As with sequential access, direct access involves a shared read–write mechanism. However, individual blocks or records have a unique address based on physical location. Access is accomplished by direct access to reach a general vicinity plus

sequential searching, counting, or waiting to reach the final location. Again, access time is variable. Disk units are direct access.

Associative: This is a random access type of memory that enables one to make a comparison of desired bit locations within a word for a specified match, and to do this for all words simultaneously. Thus, a word is retrieved based on a portion of its contents rather than its address. As with ordinary random-access memory, each location has its own addressing mechanism, and retrieval time is constant independent of location or prior access patterns. Cache memories may employ associative access.

Internal vs. External Memory


- *Internal*
 - *Semiconductor memories*
 - *Register, Cache, Main Memory*
- *External*
 - *Magnetic/ Optical/ Semiconductor*
 - *Hard disks, Optical disks, SSD*



Memory Organization

RAM vs. ROM

- Read Write Memory (RAM)
 - Misnamed as all semiconductor memory is random access
 - Read/Write
 - Volatile
 - Temporary storage
- Read Only Memory (ROM)
 - nonvolatile
 - Permanent storage

Fall 2021

Memory Definitions

8

The process of storing new information in memory is referred to as a *memory write* operation.

The process of transferring the stored information out of memory is referred to as a *memory read* operation.

Figure 7-2: Contents of a 1024×16 Memory

<u>Memory Address</u>		<u>Memory Contents</u>
<u>Binary</u>	<u>Decimal</u>	
000000000	0	10110101 01011100
000000001	1	10101011 10001001
000000010	2	00001101 01000110
	.	.
	.	.
	.	.
	.	.
111111101	1021	10011101 00010101
111111110	1022	00001101 00011110
111111111	1023	11011110 00100100


A word is an entity of bits that moves in and out of memory as a unit.
Each word in memory is assigned an identification number called an *address*.

Contents

- *Memory Definitions*
- *Random Access Memory*
 - *SRAM Integrated Circuits*
 - *Array of SRAM ICs*
 - *DRAM Integrated Circuits*
- *Read Only Memory*



Figure 7-1: Block Diagram of Memory

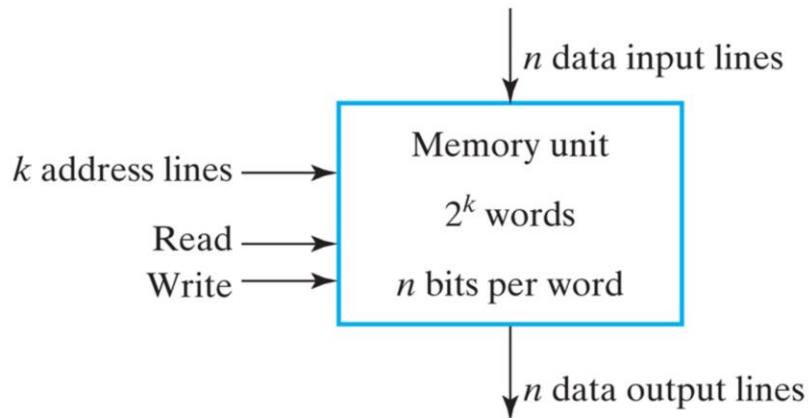

The capacity of a memory unit is usually stated as the total number of *bytes* or *bits* that it can store.

The n data input/output lines provide the information to be stored in/read from memory.

The k address lines specify the particular word chosen among the many available.

The steps that must be taken for a *write* are as follows:


1. Apply the binary address of the desired word to the address lines.
2. Apply the data bits that must be stored in memory to the data input lines.
3. Activate the Write input.

The steps that must be taken for a *read* are as follows:

1. Apply the binary address of the desired word to the address lines.
2. Activate the Read input


Table 7.1: Control Inputs to a Memory Chip

Chip Select CS	Read/Write R/W	Memory Operation
0	×	None
1	0	Write to selected word
1	1	Read from selected word

 

Memory is made up of RAM integrated circuits (chips), plus additional logic circuits.
 A *Chip Select* selects the chip to be read from or written to
 A Read/Write that determines the particular operation

Figure 7-3: Memory Cycle Timing Waveforms

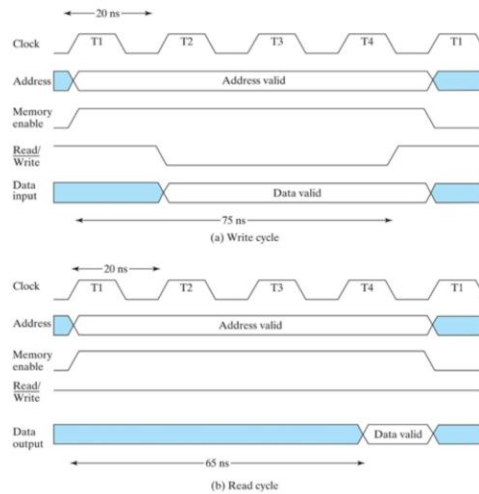

The operation of the memory unit is controlled by an external device, such as a CPU.


The *access time* of a memory read operation is the maximum time from the application of the address to the appearance of the data at the Data Output.

The *write cycle time* is the maximum time from the application of the address to the completion of all internal memory operations required to store a word.

Memory Organization

Contents

- *Memory Definitions*
- *Random Access Memory*
 - *SRAM Integrated Circuits*
 - *Array of SRAM ICs*
 - *DRAM Integrated Circuits*
- *Read Only Memory*



Fall 2021

14

Static RAM (SRAM) consists of internal latches that store the binary information. The stored information remains valid as long as power is applied to the RAM.

Dynamic RAM (DRAM) stores the binary information in the form of electric charges on capacitors. The capacitors must be periodically recharged by *refreshing* the DRAM.

Figure 7-4: Static RAM Cell


 



Figure 7-5: RAM Bit Slice Model

 

Only one word is written at a time. That is, only one Word Select line is 1, and all other Word Select lines are 0.

Each *Word Select* line extends beyond the bit slice, so that when multiple RAM bit slices are placed side by side, corresponding Word Select lines connect.

Figure 7-6: 16-Word by 1-Bit RAM Chip

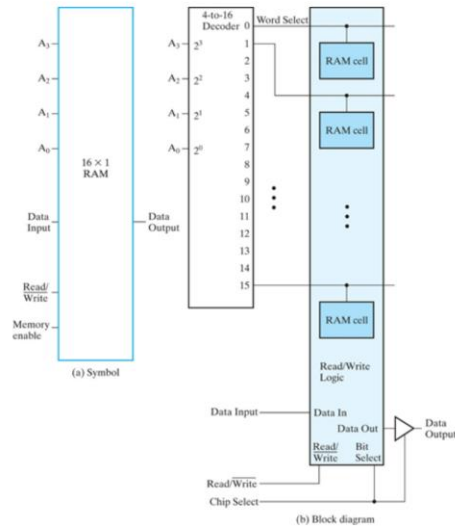


The three-state buffer allows construction of a multiplexer with an arbitrary number of inputs.

Three-state outputs are connected together and properly controlled using the Chip Select inputs.

Chip select combinations containing a single 1 can be obtained from a decoder.

Figure 7-7: Diagram of a 16×1 RAM Using a 4×4 RAM Cell Array

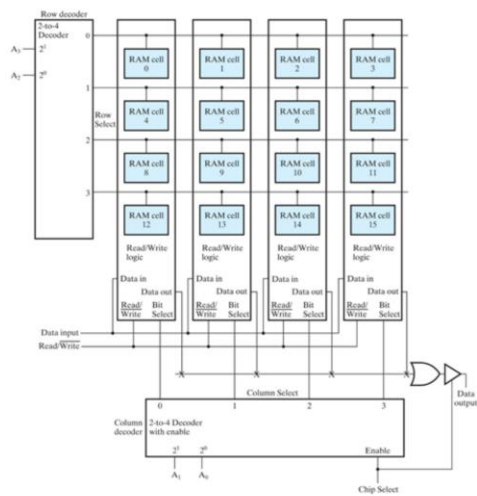


Coincident Selection

One decoder controls the word select lines (*Row Select*) and the other controls the bit select lines (*Column Select*).

The result is a two-dimensional matrix selection scheme.

The column decoder is enabled with the Chip Select input.

Figure 7-8: Block Diagram of an 8×2 RAM Using a 4×4 RAM Cell Array

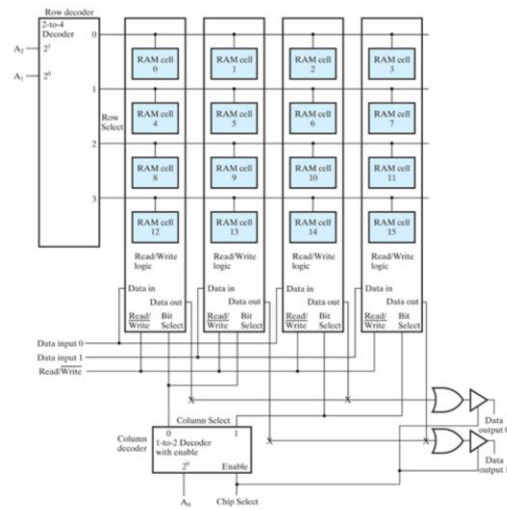


The same RAM cell array is used in Figure 7-8 to produce an 8×2 RAM chip (eight words of two bits each).

The only changes are in the column and output logic.

Memory Organization

Contents

- *Memory Definitions*
- *Random Access Memory*
 - *SRAM Integrated Circuits*
 - *Array of SRAM ICs*
 - *DRAM Integrated Circuits*
- *Read Only Memory*




Fall 2021

20

If the memory unit needed for an application is larger than the capacity of one chip, it is necessary to combine a number of chips in an array to form the required size of memory

Figure 7-9: Symbol for a 64K × 8 RAM Chip

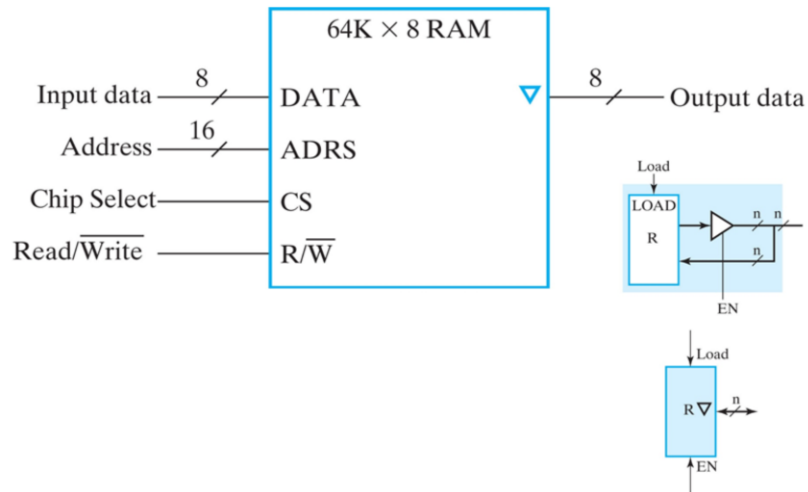

To reduce the number of pins on the chip package, many RAM ICs provide common terminals for the data input and data output.

The common terminals are said to be *bidirectional*

Figure 7-10: Block Diagram of a 256K × 8 RAM


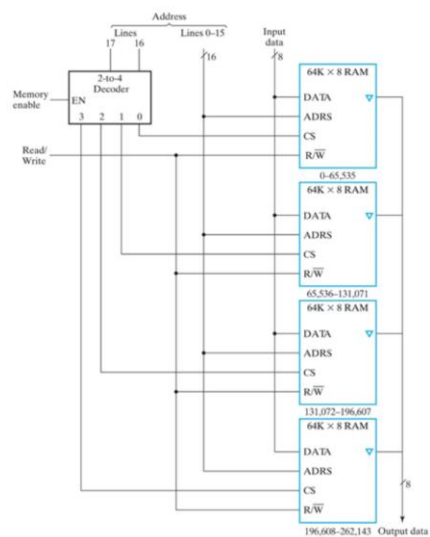


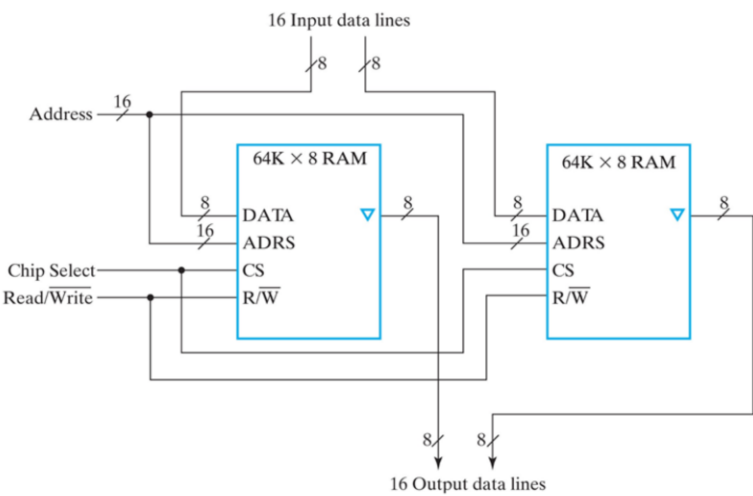

Figure 7-11: Block Diagram of a 64K × 16 RAM





Contents

- *Memory Definitions*
- *Random Access Memory*
 - *SRAM Integrated Circuits*
 - *Array of SRAM ICs*
 - *DRAM Integrated Circuits*
- *Read Only Memory*



Fall 2021

24

Memory is a collection of binary *storage* cells together with associated circuits needed to transfer information into and out of the cells.

Two types of memories are used in various parts of a computer: *random-access memory* (RAM) and *read-only memory* (ROM).

RAM accepts new information for storage to be available later for use.

The process of storing new information in memory is referred to as a *memory write* operation.


The process of transferring the stored information out of memory is referred to as a *memory read* operation.

RAM can perform both the write and the read operations, whereas ROM performs only read operations.

Memory units that lose stored information when power is turned off are said to be *volatile*.

RAMs are volatile while ROMs are *nonvolatile*.

Figure 7-12: Dynamic RAM cell, hydraulic analogy of cell operation, and cell model

 

If sufficient charge is stored on the capacitor, it can be viewed as storing a logical 1.

The transistor acts much like a switch. When the switch is “open,” the charge on the capacitor roughly remains fixed— is stored.

When the switch is “closed,” charge can flow into and out of the capacitor from the external Bit (B) line. This charge flow allows the cell to be written with a 1 or 0 and to be read.

Destructive read: the read operation destroys the stored value

Figure 7-13: DRAM Bit-Slice Model


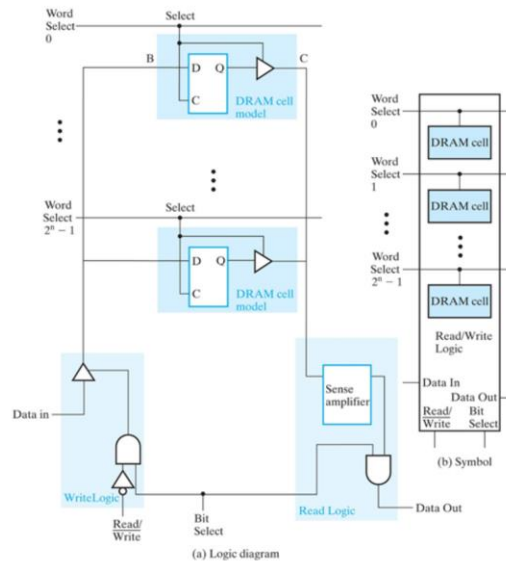


Figure 7-14: Block Diagram of a DRAM Including Refresh Logic

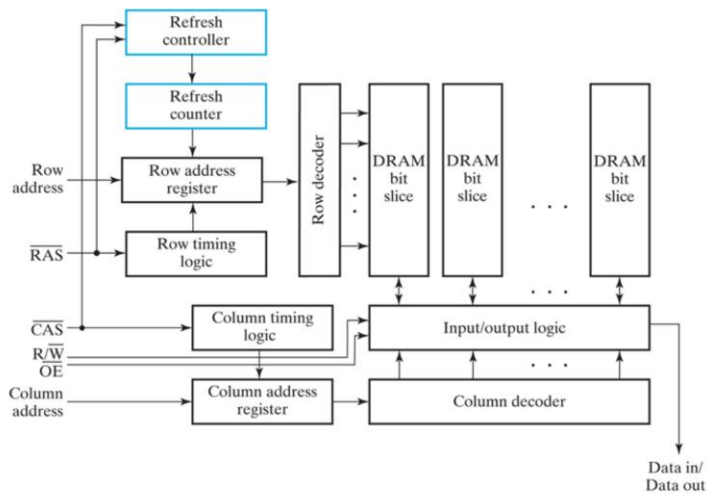


To reduce the number of pins, the DRAM address is applied serially in two parts with the row address first and the column address second.

RAS: Row address Strobe

CAS: Column Address Strobe


Figure 7-15: Timing for DRAM Write and Read Operations

 

Memory Organization

Contents

- *Memory Definitions*
- *Random Access Memory*
 - *SRAM Integrated Circuits*
 - *Array of SRAM ICs*
 - *DRAM Integrated Circuits*
- *Read Only Memory*



Fall 2021


29

Two types of memories are used in various parts of a computer: *random-access memory* (RAM) and *read-only memory* (ROM).

RAM can perform both the write and the read operations, whereas ROM performs only read operations.

RAMs are volatile while ROMs are *nonvolatile*.

Figure 5-7 Block Diagram and Internal Logic of a ROM

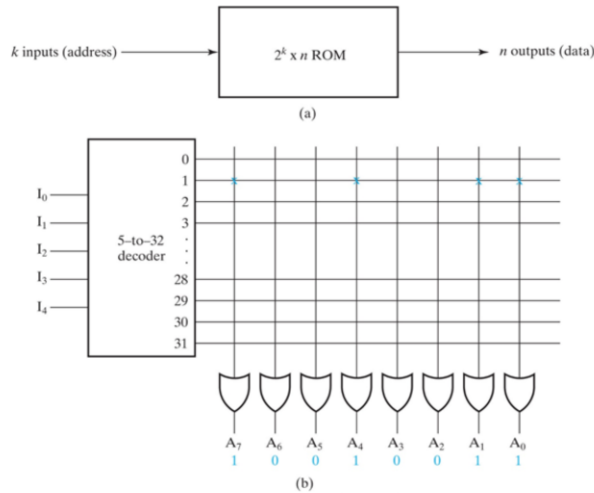

Read-only memories have different names:

1. ROM: mask programmed,
2. PROM: fuse or anti-fuse programmed,
3. EPROM: erasable floating gate programmed,
4. EEPROM or E2PROM: electrically erasable floating gate programmed,
5. FLASH Memory: electrically erasable floating gate with multiple erasure and programming modes.

The choice of programming technology depends on many factors, including the number of identical ROMs to be produced, the desired permanence of the programming, the desire for reprogrammability, and the desired performance in terms of delay

Summary: Random Access Memory Types

Memory Type	Category	Erasure	Write Mechanism	Volatility
Random-access memory (RAM)	Read-Write Memory (RWM)	Electrically, byte-level	Electrically	Volatile
Read-only memory (ROM)	Read-Only Memory (ROM)	Not possible	Masks	Nonvolatile
Programmable ROM (PROM)			Electrically	
Erasable PROM (EPROM)	Read-Mostly Memory (RMM)	UV light, chip-level		
Electrically Erasable PROM (EEPROM)		Electrically, byte-level		
Flash memory		Electrically, block-level		

